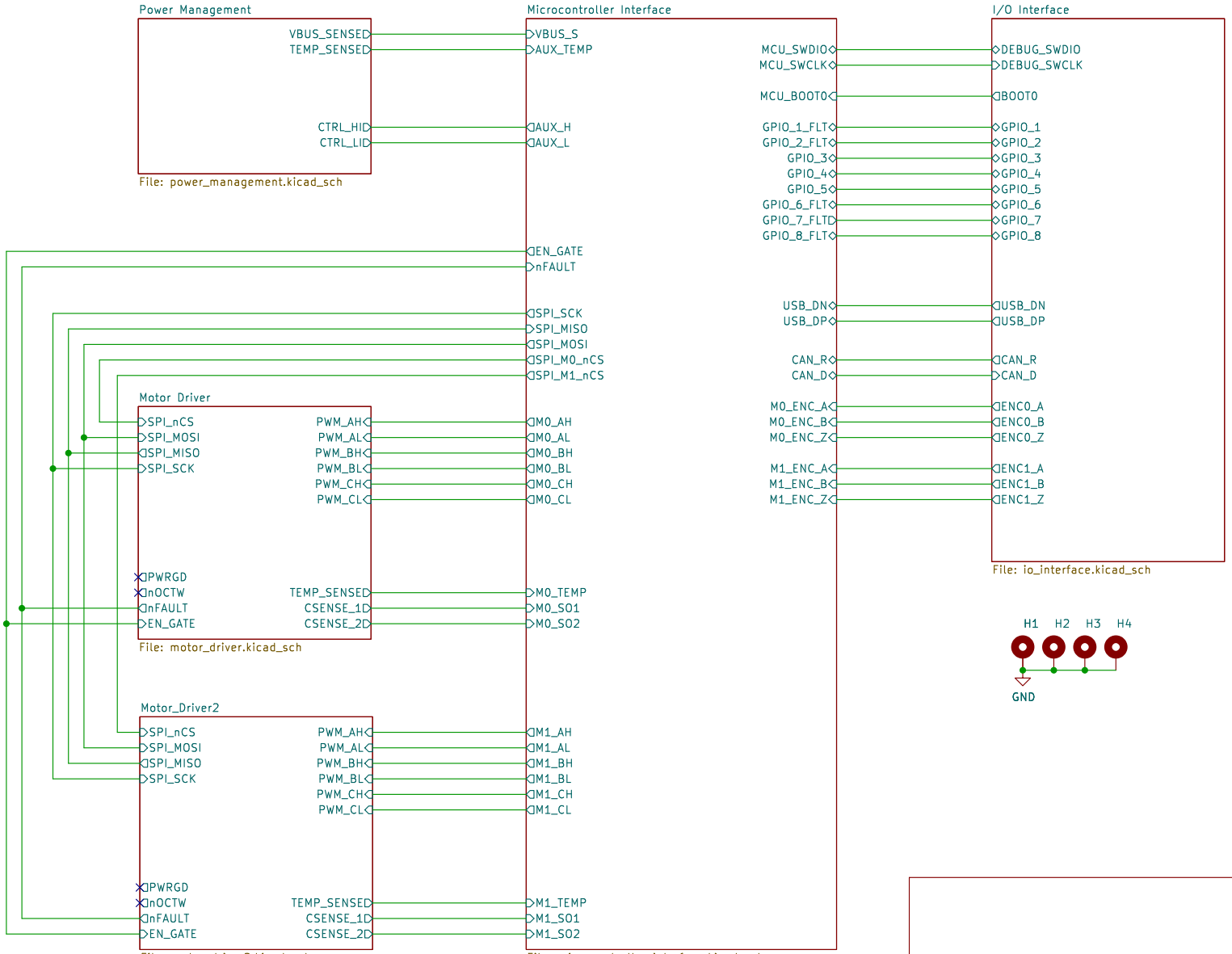

Dj140

Sheet: /

File: bldc_motor_cntroller.kicad_sch

Title: X_Odrive

Size: A4	Date: 2021-03-25	**Rev: 1.0.0**
KiCad E.D.A. 9.0.7		Id: 1/6

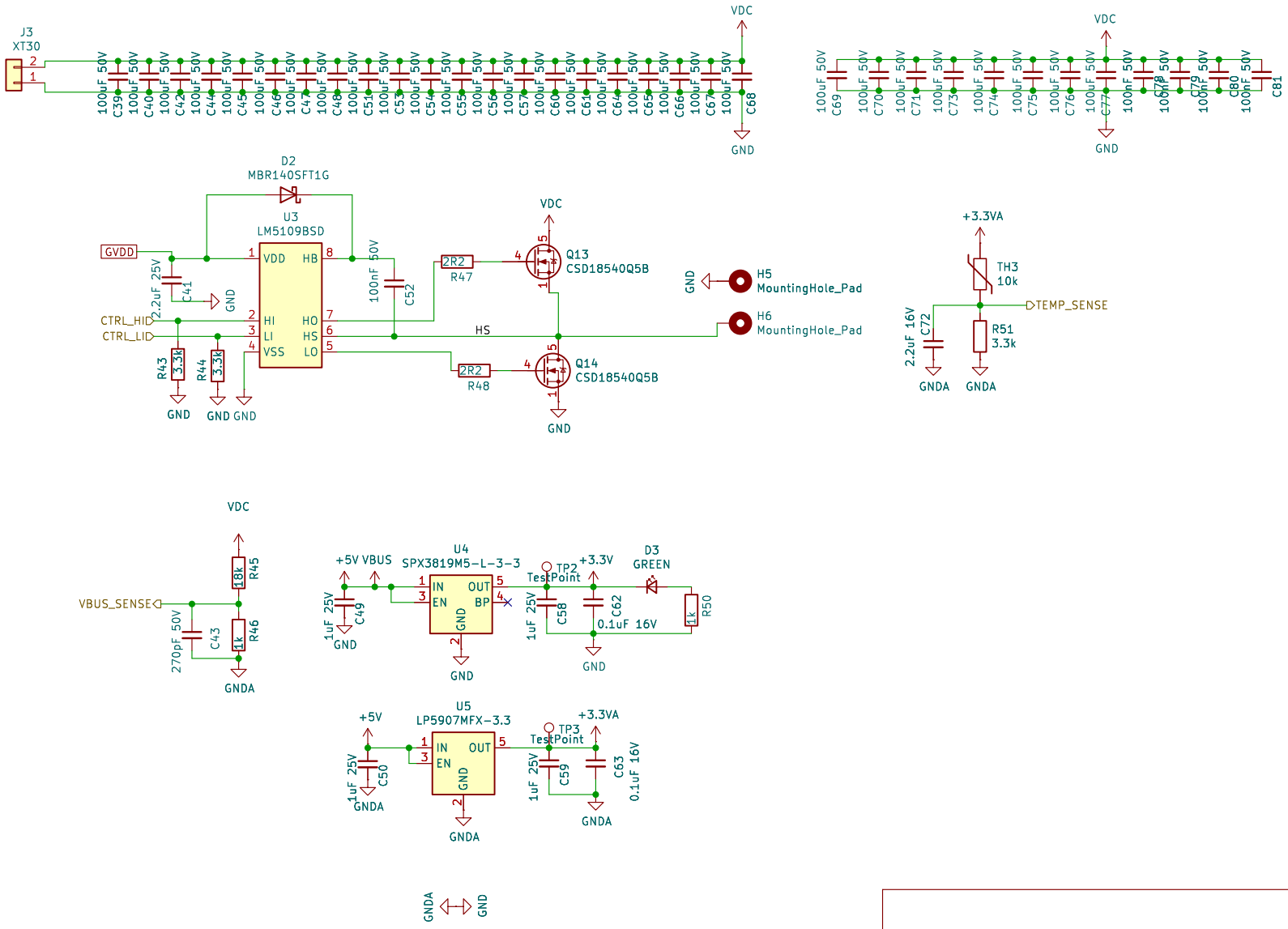

Dj140		
Sheet: /Power Management/		
File: power_management.kicad_sch		
Title: Power Management		
Size: A4	Date: 2021-03-25	**Rev: 1.0.0**
KiCad E.D.A. 9.0.7		Id: 2/6

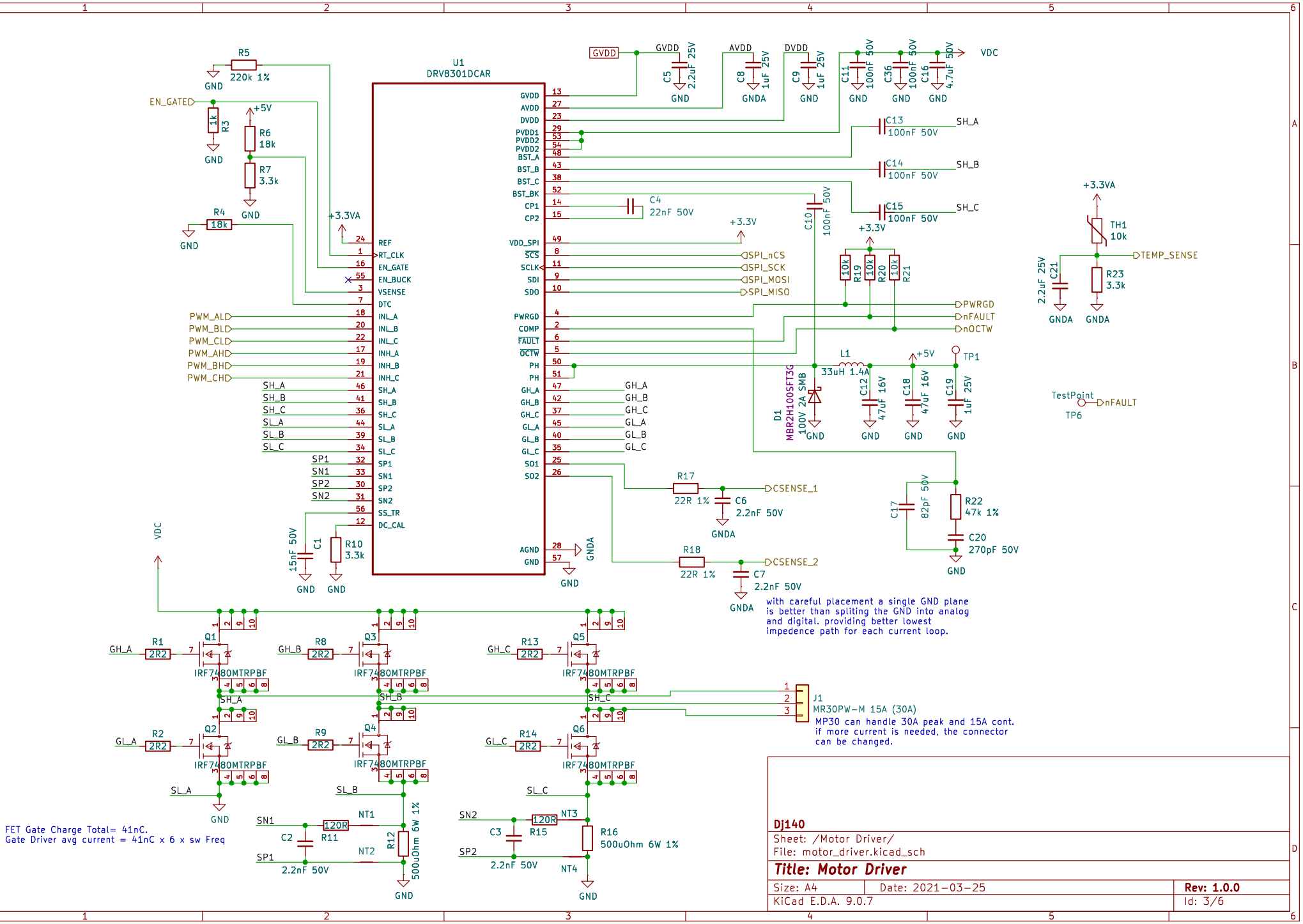
U1
DRV8301DCAR
R5
220k 1%
R6
18k
R7
3.3k
R4
18k
R3
1k
EN_GATE
+5V
+3.3VA
GND
PWM_ALD
PWM_BLD
PWM_CLD
PWM_AHD
PWM_BHD
PWM_CHD
SH_A
SH_B
SH_C
SL_A
SL_B
SL_C
SP1
SN1
SP2
SN2
C1
15nF 50V
R10
3.3k
GVDD
AVDD
DVDD
C5
2.2uF 25V
C8
1uF 25V
C9
1uF 25V
C11
100nF 50V
C36
100nF 50V
C16
4.7uF 50V
VDC
C13
100nF 50V
C14
100nF 50V
C15
100nF 50V
C4
22nF 50V
C10
100nF 50V
+3.3V
SPI_nCS
SPI_SCK
SPI_MOSI
SPI_MISO
R19
10k
R20
10k
R21
10k
PWRGD
nFAULT
nOCTW
L1
33uH 1.4A
+5V
TP1
D1
MBR2H100SFT3G
100V 2A SMB
C12
47uF 16V
C18
47uF 16V
C19
1uF 25V
GH_A
GH_B
GH_C
GL_A
GL_B
GL_C
R17
22R 1%
C6
2.2nF 50V
GNDA
R18
22R 1%
C7
2.2nF 50V
CSENSE_1
CSENSE_2
C17
82pF 50V
R22
47k 1%
C20
270pF 50V
TH1
10k
R23
3.3k
C21
2.2uF 25V
TEMP_SENSE
TestPoint
TP6
nFAULT
with careful placement a single GND plane
is better than spliting the GND into analog
and digital. providing better lowest
impedence path for each current loop.
Q1
Q2
Q3
Q4
Q5
Q6
IRF7480MTRPBF
R1
R2
R8
R9
R13
R14
2R2
J1
MR30PW-M 15A (30A)
MP30 can handle 30A peak and 15A cont.
if more current is needed, the connector
can be changed.
NT1
NT2
NT3
NT4
120R
R11
R12
R15
R16
500uOhm 6W 1%
C2
2.2nF 50V
C3
2.2nF 50V
FET Gate Charge Total= 41nC.
Gate Driver avg current = 41nC x 6 x sw Freq
Dj140
Sheet: /Motor Driver/
File: motor_driver.kicad_sch
Title: Motor Driver
Size: A4
Date: 2021-03-25
Rev: 1.0.0
KiCad E.D.A. 9.0.7
Id: 3/6

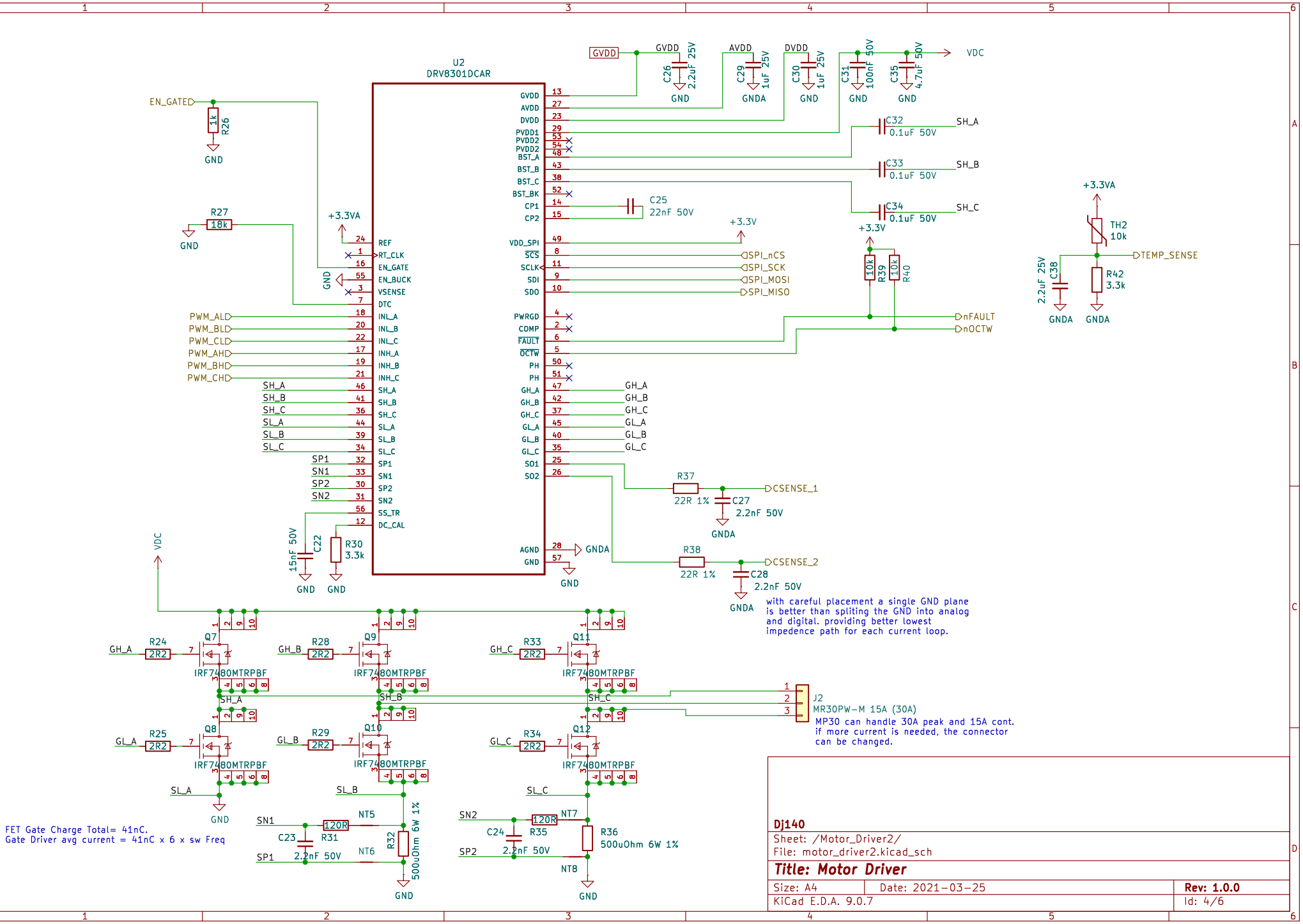
U2
DRV8301DCAR
GVDD
AVDD
DVDD
VDC
C26 2.2uF 25V
C29 1uF 25V
C30 1uF 25V
C31 100nF 50V
C35 4.7uF 50V
GND
GNDA
EN_GATE
R26 1k
R27 18k
+3.3VA
C25 22nF 50V
+3.3V
C32 0.1uF 50V
C33 0.1uF 50V
C34 0.1uF 50V
SH_A
SH_B
SH_C
TH2 10k
R42 3.3k
C38 2.2uF 25V
TEMP_SENSE
R39 10k
R40 10k
nFAULT
nOCTW
SPI_nCS
SPI_SCK
SPI_MOSI
SPI_MISO
PWM_ALD
PWM_BLD
PWM_CLD
PWM_AHD
PWM_BHD
PWM_CHD
R37 22R 1%
C27 2.2nF 50V
CSENSE_1
R38 22R 1%
C28 2.2nF 50V
CSENSE_2
C22 15nF 50V
R30 3.3k
with careful placement a single GND plane is better than spliting the GND into analog and digital. providing better lowest impedence path for each current loop.
Q7
Q8
Q9
Q10
Q11
Q12
IRF7480MTRPBF
R24 2R2
R25 2R2
R28 2R2
R29 2R2
R33 2R2
R34 2R2
J2
MR30PW-M 15A (30A)
MP30 can handle 30A peak and 15A cont. if more current is needed, the connector can be changed.
R31 120R
R32 500uOhm 6W 1%
R35 120R
R36 500uOhm 6W 1%
C23 2.2nF 50V
C24 2.2nF 50V
NT5
NT6
NT7
NT8
FET Gate Charge Total= 41nC.
Gate Driver avg current = 41nC x 6 x sw Freq
Dj140
Sheet: /Motor_Driver2/
File: motor_driver2.kicad_sch
Title: Motor Driver
Size: A4
Date: 2021-03-25
Rev: 1.0.0
KiCad E.D.A. 9.0.7
Id: 4/6

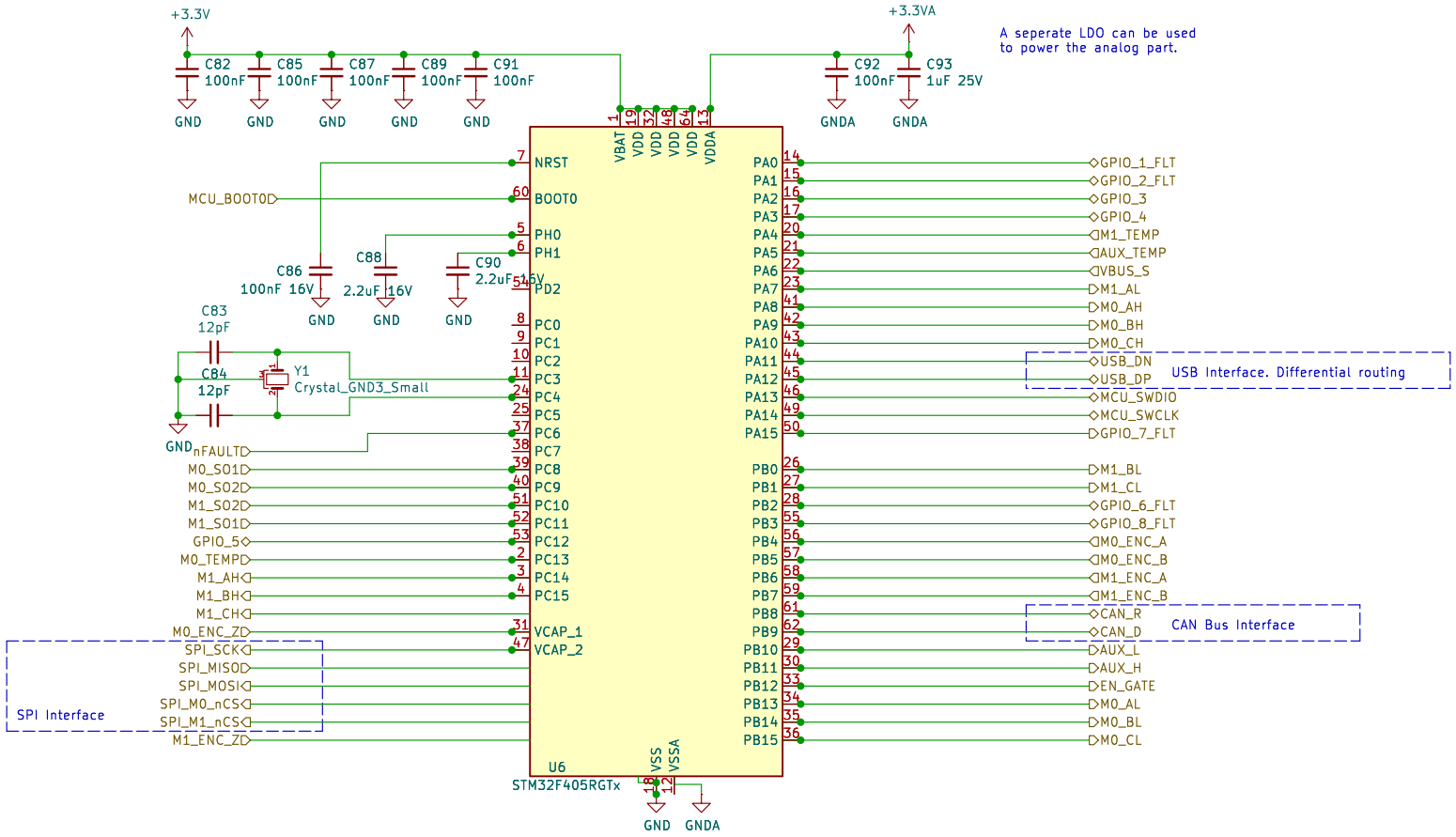

Dj140		
Sheet: /Microcontroller Interface/		
File: microcontroller_interface.kicad_sch		
Title: Microcontroller Interface		
Size: A4	Date: 2021-03-25	**Rev: 1.0.0**
KiCad E.D.A. 9.0.7		Id: 5/6

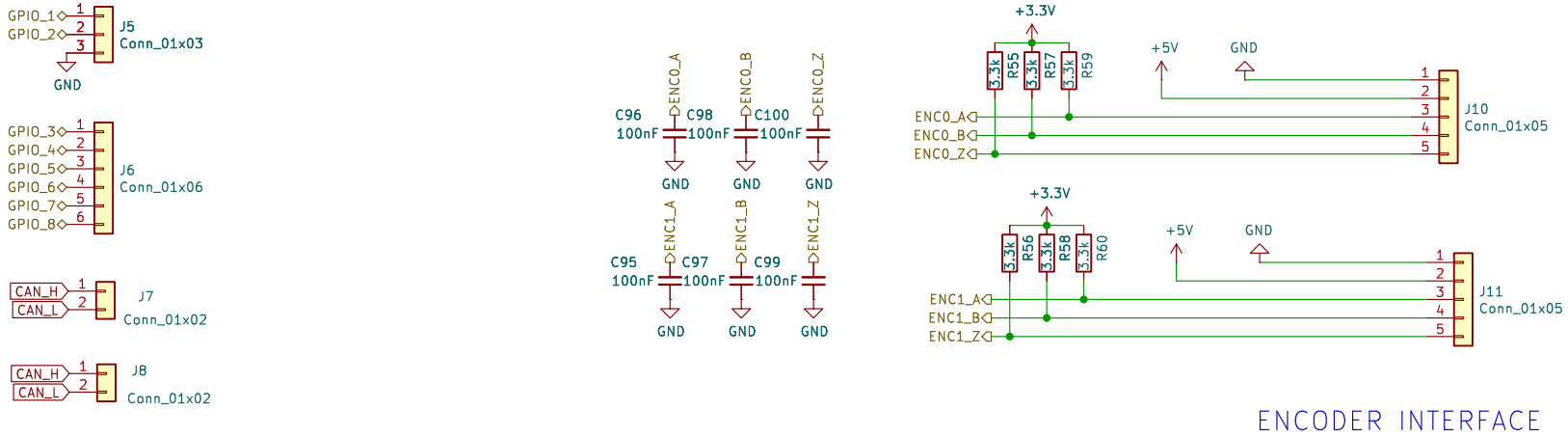

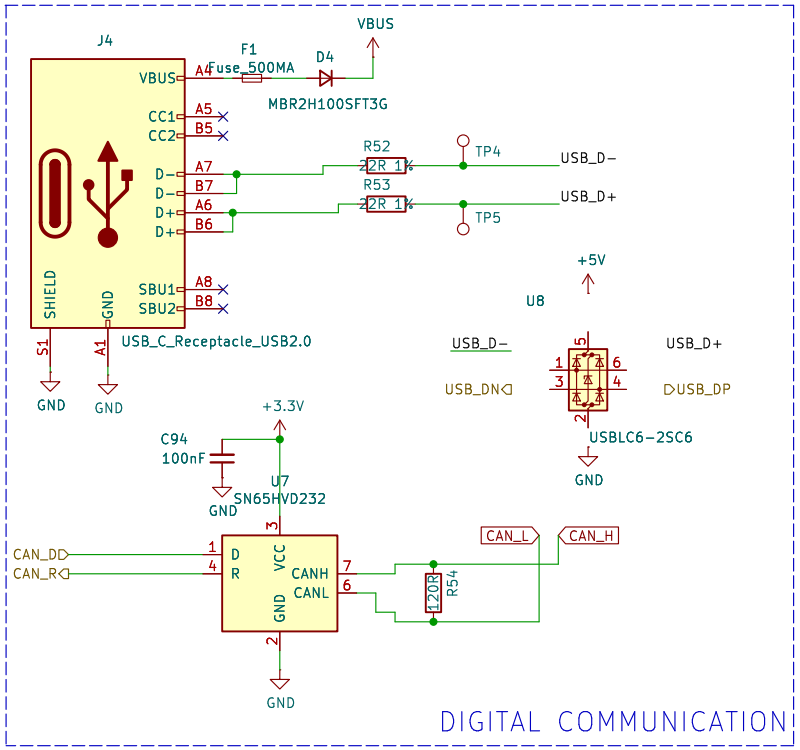

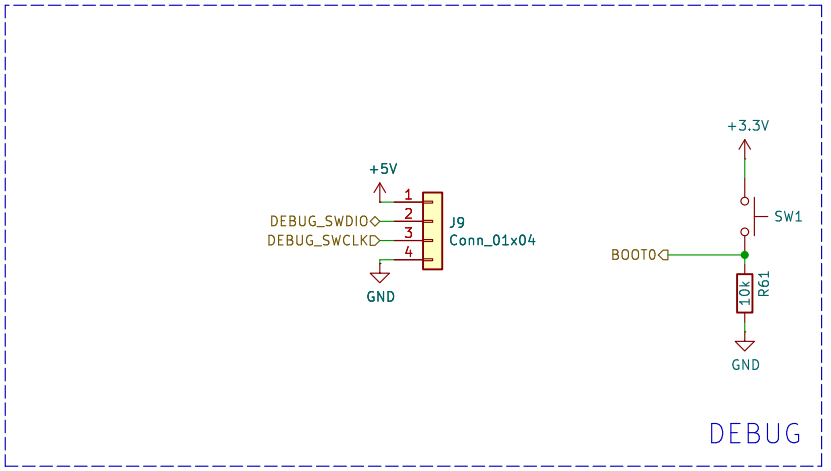

Dj140		
Sheet: /I/O Interface/		
File: io_interface.kicad_sch		
Title: I/O Interface		
Size: A4	Date: 2021-03-25	**Rev: 1.0.0**
KiCad E.D.A. 9.0.7		Id: 6/6